



0-WEB.ru

[Alternating current circuits corcoransolutionpdfdownload](#)

Chapter-1
Network Concepts

1.1 Given

There branch voltages are, $v_{b1} = (-2 + 3i_{b2})$
 $v_{b2} = (-4 + 2i_{b2})$
 $v_{b3} = 2i_{b3}$

(a) Using mesh analysis (mesh - 1)

$$i_2 (2 + 2) + i_1 (2) = 4$$

or, $i_2 (4) + i_1 (2) = 4$ (i)

Using mesh analysis. (mesh - 2)

$$i_1 (2 + 2 + 1) + i_2 (2) = 2$$

or, $5i_1 + 2i_2 = 2$ (ii)

If i_{b1}, i_{b2}, i_{b3} are the independent variable,

$$i_2 = i_{b2}$$

$$i_{b3} = i_1 + i_2 \quad \text{or, } i_2 = i_{b3} - i_{b1}$$

$$i_{b1} = i_1$$

So equation (i) and (ii) can be written as,

$$2i_2 + i_1 = 2$$

or, $2i_{b2} + i_{b1} = 2$

and $5i_1 + 2i_2 = 2$

or, $5i_{b1} + 2i_{b2} = 2$


Thus,

$$i_{b3} = i_1 + i_2$$

$$2i_{b2} + i_{b1} = 2$$

$$5i_{b1} + 2i_{b2} = 2$$

1.2

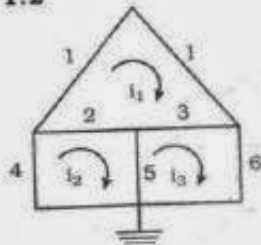

Given, branch resistance,

$$R_{b1} = 2, R_{b2} = 2, R_{b3} = 3, R_{b4} = 4$$

$$R_{b5} = 5, R_{b6} = 6 \text{ ohms}$$



0-WEB.ru

3bd2c15106